



Udemy Sequential Lab

[sequential - Google](#) 雲端硬碟

serial2parallel、parallel2serial、combinational_lock、vending_machine

第4組 2023.8.16

| C code » Verilog

1. Add clock and reset signal

```
void c_code(  
    bool a,  
    ap_int<8> b,  
  
    bool &c,  
    int &d)  
{  
  
}
```

C code in HLS

- Add signal automatically

```
module verilog(  
    input clk,  
    input rst_n,  
  
    input a,  
    input [7:0] b,  
  
    output c,  
    output [31:0] d  
);  
  
endmodule
```

Verilog in Vivado

- Add signal by self

| C code >> Verilog

2. Notice pragma in HLS

- Interface

```
#pragma HLS INTERFACE ap_none port=a  
#pragma HLS INTERFACE ap_vld port=a
```

- Unroll

```
#pragma HLS UNROLL
```


- Pipeline

```
#pragma HLS PIPELINE
```

- Others

C code » Verilog

3. Choose wire or reg in Verilog

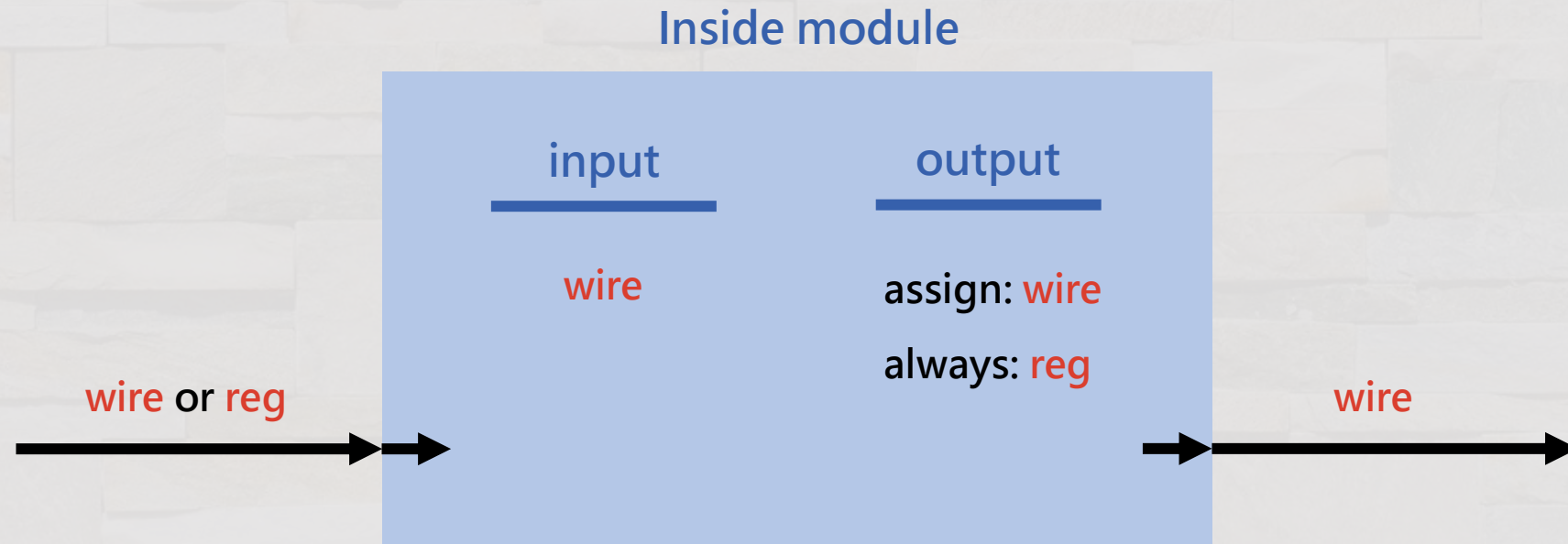

C code » Verilog

4. Sequential circuit typing style

```
static bool a = 0;
bool next_a;

// Combinational Part
if(a == 0)
    next_a = 1;
else
    next_a = 0;

// Sequential Part
a = next_a;
```

C code in HLS

- Sequential part is later

```
reg a = 0;
reg next_a;

// Combinational Part
always @(*)
begin
    if(a == 0)
        next_a = 1;
    else
        next_a = 0;
end

// Sequential Part
always @(posedge clk or negedge rst_n)
begin
    if(!rst_n)
        a <= 0;
    else
        a <= next_a;
end
```

Verilog in Vivado


- Sequential part use non-blocking

serial2parallel

FSM design

Lab 1

■ Design a counter count from 0-8

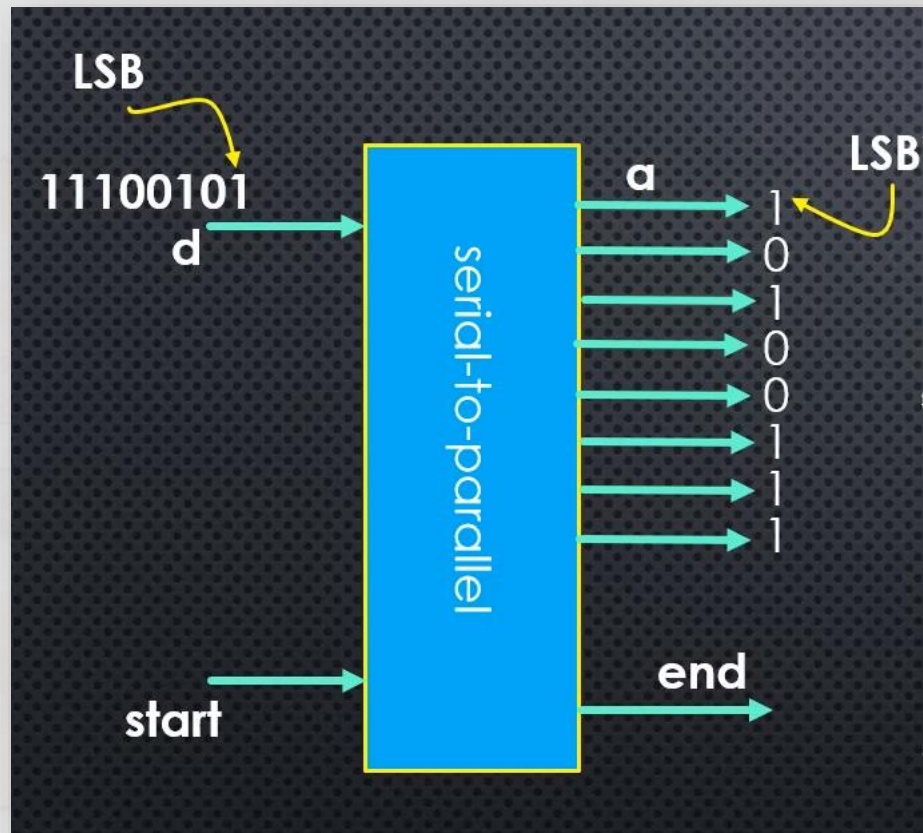

serial2parallel

Lab 1

Coding

■ Testbench

```
module serial2parallel_tb();

reg clk, rst_n, d, start_serial_data;
reg [7:0] data = 8'b01001101;
wire end_conversion;
wire [7:0] a;

serial2parallel S0 (.clk(clk), .rst_n(rst_n),
                   .serial_start(start_serial_data), .d(d),
                   .end_conversion(end_conversion), .a(a));

always #10 clk = ~clk;

initial begin

    clk = 0;
    start_serial_data = 0;
    $display("=== Initialize Success ===");
```

```
    rst_n = 1;
    #10 rst_n = 0;
    #10 rst_n = 1;
    $display("=== Reseting ===");

    #30 start_serial_data = 1;
    for(integer i = 0; i < 8; i = i + 1)
    begin
        d = data[i];
        #20 start_serial_data = 0;
    end
    $display("=== Test Result ===");
    #20 $display("a = %b", a);

    if(a == data)
        $display("=== Test Passed ===");
    else
        $display("=== Test Failed ===");

end


endmodule
```

serial2parallel

Lab 1

Coding

■ Simulation result

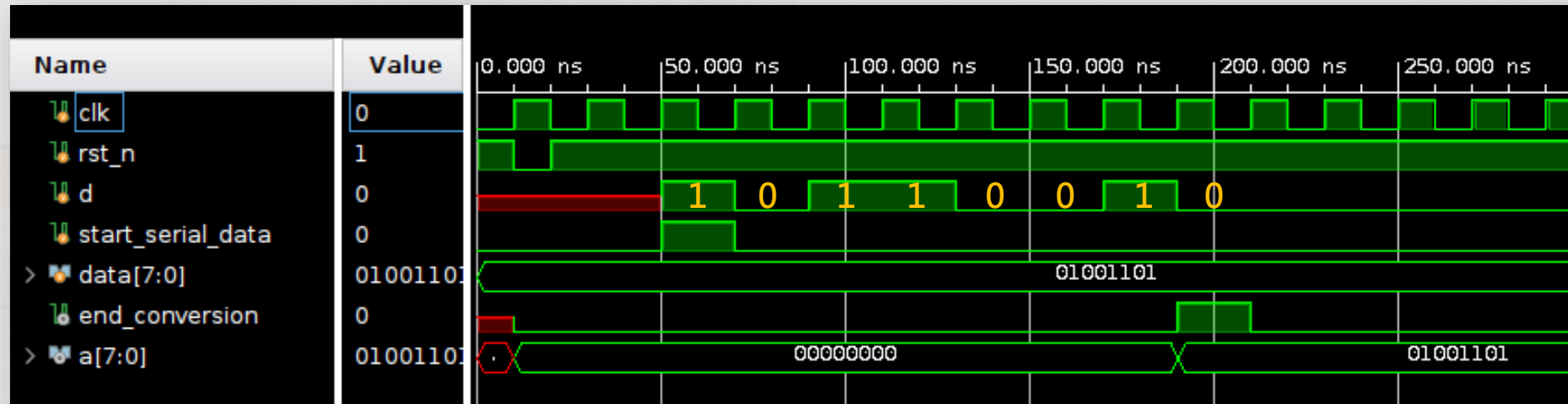

■ Compare to HLS

	FF	LUT	Timing
HLS	49	163	5.140 ns
Vivado	28	11	0 ns


Design Runs Timing x			
Design Timing Summary			
Setup		Hold	
Worst Negative Slack (WNS):	inf	Worst Hold Slack (WHS):	inf
Total Negative Slack (TNS):	0.000 ns	Total Hold Slack (THS):	0.000 ns
Number of Failing Endpoints:	0	Number of Failing Endpoints:	0
Total Number of Endpoints:	61	Total Number of Endpoints:	61
There are no user specified timing constraints.			

parallel2serial

FSM design

Lab 2

■ Design a counter count from 0-8

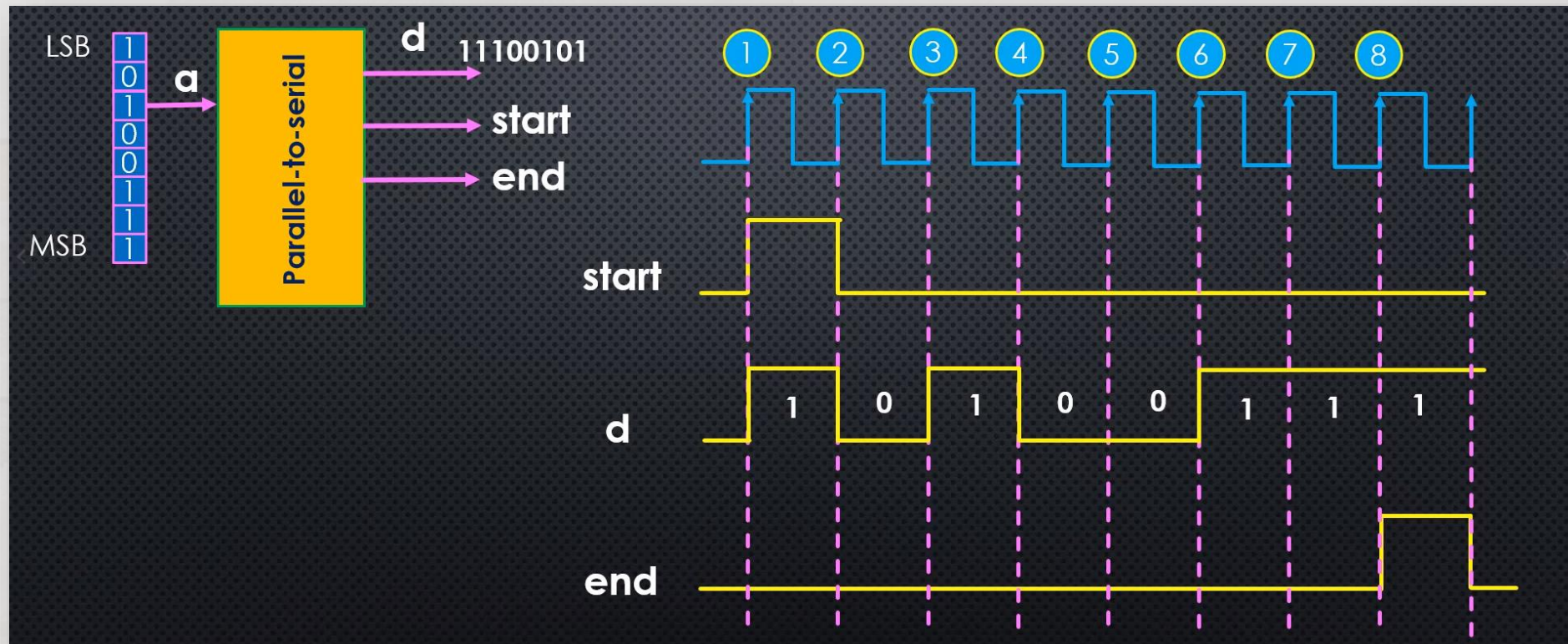

parallel2serial

Lab 2

Coding

■ Testbench

```
module parallel2serial_tb();

    reg clk, rst_n, bgn;
    reg [7:0] in_parallel = 8'b11010011, out_serial;
    wire serial_start, serial_end, d;

    parallel2serial P0 (.clk(clk), .rst_n(rst_n), .a(in_parallel), .bgn(bgn),
                      .d(d), .serial_start(serial_start), .serial_end(serial_end));

    always #10 clk = ~clk;

    initial begin
        clk = 0;
        bgn = 0;
        $display("=== Initialize Success ===");
    end
endmodule
```


```
        rst_n = 1;
        #10 rst_n = 0;
        #10 rst_n = 1;
        $display("=== Resetting ===");

        $display("=== Test Result ===");
        #30 bgn = 1;
        for(integer i = 0; i < 8; i = i + 1)
            begin
                #20 bgn = 0;
                out_serial[i] = d;
                $display("When i = %ld:", i);
                $display("d = %b, serial_start = %b, serial_end = %b", d, serial_start, serial_end);
            end
        #20 $display("out_serial = %b", out_serial);

        if(in_parallel == out_serial)
            $display("=== Test Passed ===");
        else
            $display("=== Test Failed ===");

    end
endmodule
```


■ Simulation result

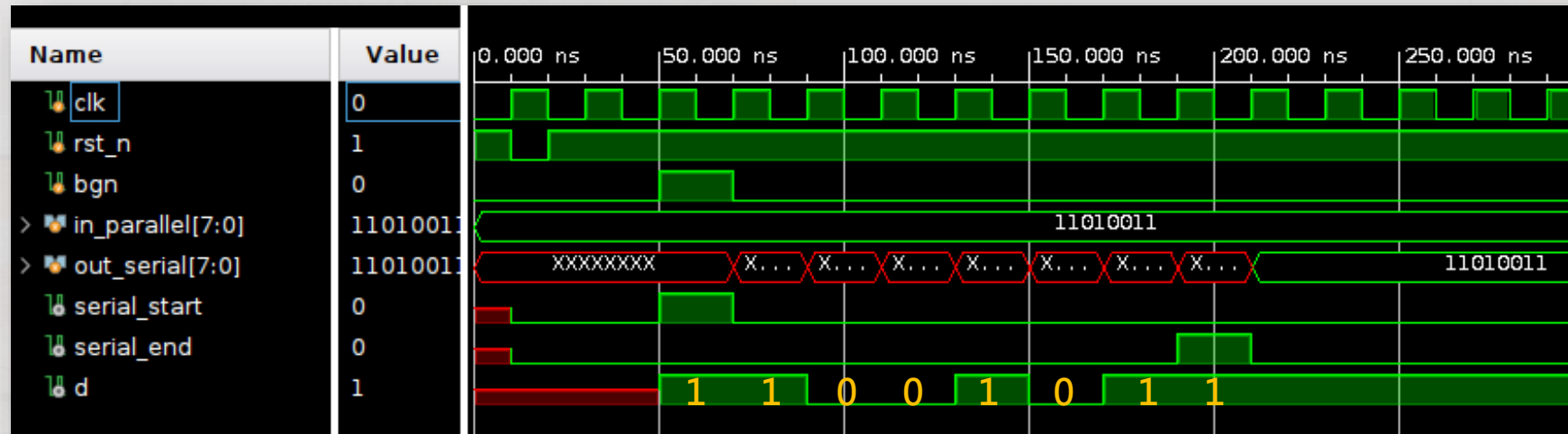

■ Compare to HLS


	FF	LUT	Timing
HLS	33	151	5.055 ns
Vivado	7	8	0 ns

combinational_lock

FSM design

Lab 3

 - **Moore machine: Door open only in s2346**




- **Use 7-segment to display states**

combinational_lock Coding

Lab 3

■ Simulation result

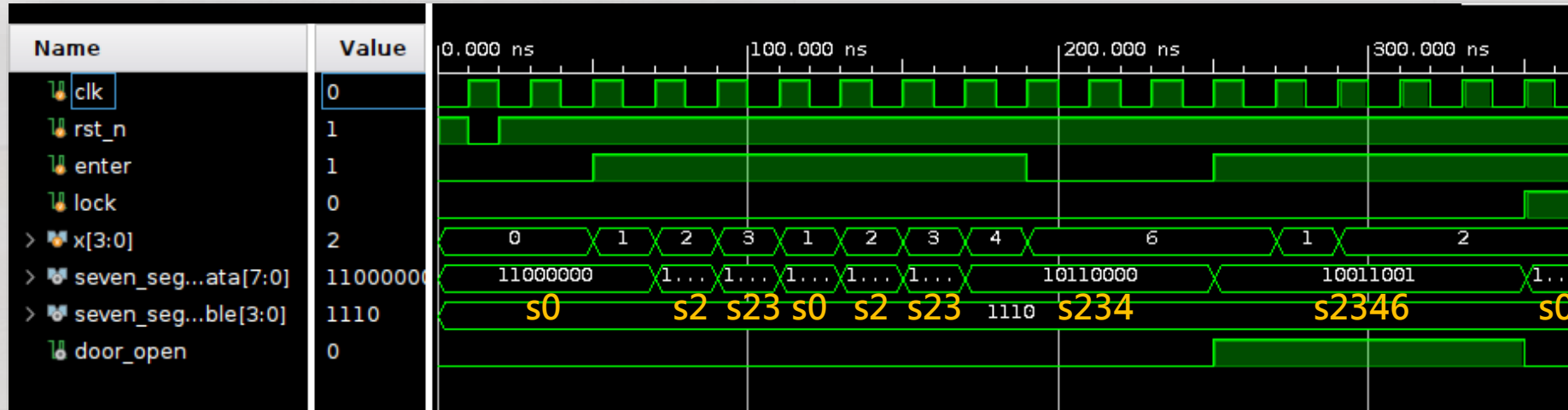

■ Compare to HLS


	FF	LUT	Timing
HLS	8	220	6.202 ns
Vivado	4	11	0 ns

vending_machine

Lab 4

FSM design

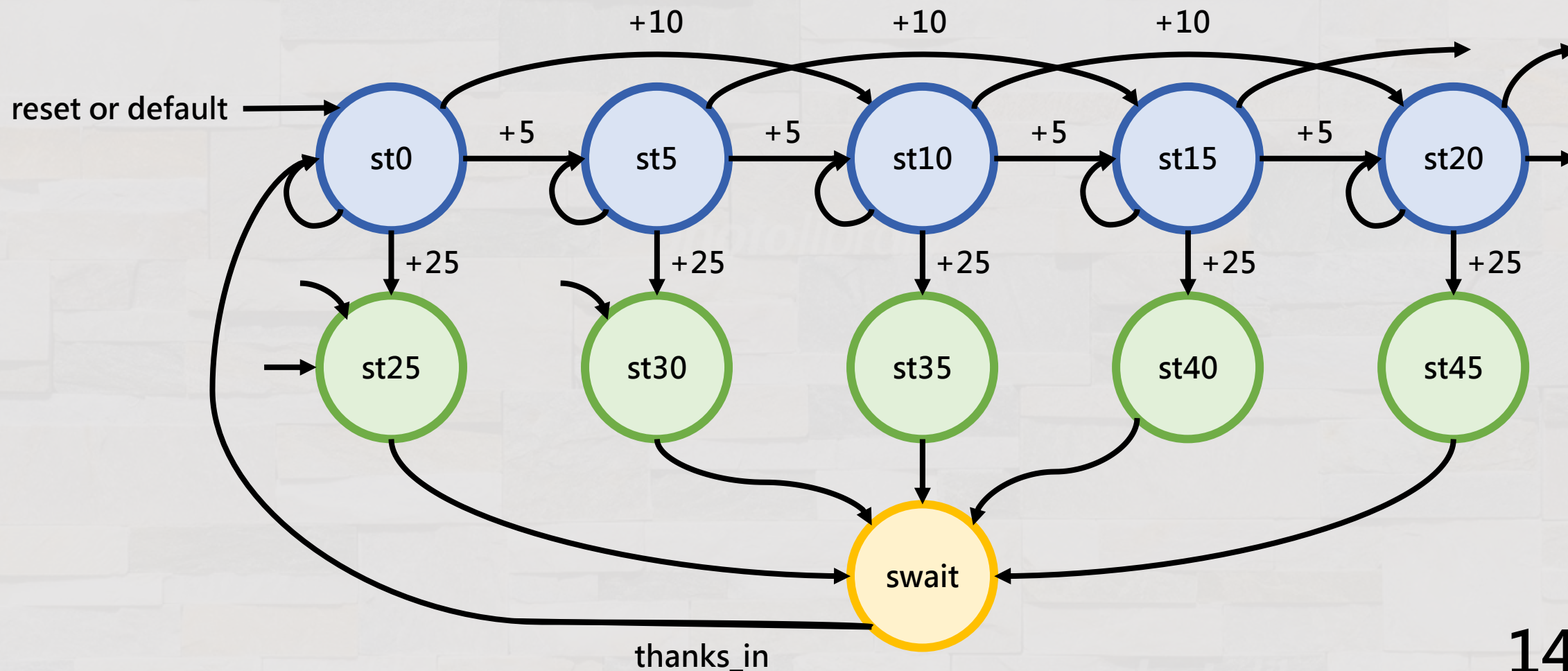■ **Moore machine: Make change only in st25 - st45**



vending_machine

Lab 4

Coding

■ Testbench

```
#30 $display("=== Test Result ===");
put_coin(0, 0, 0); // no coin
put_coin(0, 1, 0); // dime
put_coin(0, 1, 0); // dime
put_coin(0, 0, 1); // quarter

$display("=== Test Finished ===");
$finish;

end

endmodule
```

```
task put_coin;
    input nickel_in_num, dime_in_num, quarter_in_num;

    begin
        #20
        nickel_in = nickel_in_num;
        dime_in = dime_in_num;
        quarter_in = quarter_in_num;

        if(nickel_in)
            $display("Put 1 nickel inside: +5 $");
        else if(dime_in)
            $display("Put 1 dime inside: +10 $");
        else if(quarter_in)
            $display("Put 1 quarter inside: +25 $");
        else
            $display("Don't put any coins");

        $display("candy_out = %b, nickel_out = %b, dime_out = %b", candy_out, nickel_out, dime_out);
        $display("=====");

        #20
        nickel_in = 0;
        dime_in = 0;
        quarter_in = 0;

        for(integer i = 0; i < 3; i = i + 1)
            begin
                #20
                $display("Waiting...");
                $display("candy_out = %b, nickel_out = %b, dime_out = %b", candy_out, nickel_out, dime_out);
                $display("=====");
            end
    end

end


endtask
```

vending_machine

Coding

Lab 4

■ Simulation result

 

■ Compare to HLS

	FF	LUT	Timing
HLS	33	142	3.935 ns
Vivado	15	12	0 ns

Question

① Whether use pipeline design in Lab 3 ?

	FF	LUT	Timing
Pipeline	9	208	6.202 ns
No pipeline	8	220	6.202 ns

② Glitches will appear in HLS design sometimes

